

Computer and VLSI design

Control, finite state machines, microprogramming


P.J. Drongowski
SandSoftwareSound.net

Control implementation styles


- Finite state machine (FSM)
 - "Random logic" or "hardwired" approach
 - Draw state diagram for ISA instruction interpretation
 - Perform state assignment
 - Define state table
 - Implement sequential logic circuit
 - Implementation is usually ill-structured and not regular
 - PLA can make design more regular and structured
- Microprogramming
 - Each control step can be represented as an instruction
 - These control instructions can be stored in a memory
 - Technique developed by Maurice Wilkes in 1951
 - Terminology
 - ◊ Microprogram
 - ◊ Microinstruction
 - ◊ Emulation (interpeter for the ISA)
 - Control store
 - ◊ Microprogram memory
 - ◊ May be writeable (not just read-only)
 - ◊ Update to correct errors
- Two styles of microprogramming
 - Vertical
 - Horizontal

Random logic controller

- Consider the state diagram below

 

- Four state machine
 - Fetch state - get instruction from memory
 - Decode state - decode new instruction
 - Execute state - execute decoded instruction
 - Interrupt state - perform trap sequence
- Signal "Int" is an external input
 - Signal is asserted when an interrupt is requested
 - Go to Interrupt state if asserted
 - Otherwise, go to Decode state
- First step in controller design is state assignment
 - Fetch \Rightarrow 0
 - Decode \Rightarrow 1
 - Interrupt \Rightarrow 2
 - Execute \Rightarrow 3
- Redraw the state diagram with states assigned
- Assume two flip / flop (bit) representation of state

 


State table form

- After state assignment, build equivalent state table
- Each row in table represents:
 - Current machine state, and
 - Condition input combination

State	Int	S1	S0
0	0	0	0
0	1	0	0
1	X	0	1
2	X	1	0
3	X	1	1

- S1 and S1 represent high and low bit of the machine state
- "X" terms denote "don't care" condition
- Don't care terms specify input conditions to be ignored
- Each row will become a product term
 - $\sim\text{Int} \wedge \sim\text{S1} \wedge \sim\text{S0}$ (First row term)
 - $\text{Int} \wedge \sim\text{S1} \wedge \sim\text{S0}$ (Second row term)
 - $\sim\text{S1} \wedge \text{S0}$ (Third row term)
 - $\text{S1} \wedge \sim\text{S0}$ (Fourth row term)
 - $\text{S1} \wedge \text{S0}$ (Fifth row term)
- Note that ignored inputs don't appear in product term
- The product term will enable the rest of the table

 


Filling out the table

- For a given state and input:
 - Select a next state value
 - Generate control signals to datapath

State	Int	S1	S0	Next1	Next0	Control
0	0	0	0	0	1	1010101
0	1	0	0	1	0	0001100
1	X	0	1	1	1	0100101
2	X	1	0	0	0	0111110
3	X	1	1	0	0	1110001

 - Next state values are feed back through state flip / flops
- Next1, Next0, Control outputs are formed by OR logic



- Inputs to the table are variables in product terms (AND)
- Outputs are formed by OR'ing across columns
- Thus, each output signal is a sum of products expression
- Programmable logic array (PLA)
- The table can be implemented directly in a PLA

Finite state machines


- Common class of computations
- State table is one possible representation
- Each row in table contains
 - Current inputs
 - Current machine state
 - Next machine state
 - New outputs

Inputs A B C	This state	Next state	Outputs X Y
LLX	S0	S1	LL
HHX	S0	S2	LH
XXX	S1	S2	LH
XX	S2	S3	HL
XXL	S3	S3	HL
XXH	S3	S1	HH

- Operation
 - Find row matching current state and inputs
 - Treat X as a "don't care" - ignore that input
 - Assert the specified output values
 - Go to the next state making it the new current state
 - Iterate

Alternate representations

 - State diagram
 - States are represented by labelled circles
 - An arc shows transition from one state to another
 - Arcs are labelled with inputs / outputs



- Pseudo-code

```

input ABC
output XY
states S0, S1, S2, S3
  
```


```

S0: if ABC = LLX then XY := LL ; goto S1
    if ABC = HHX then XY := LH ; goto S2
S1: XY := LH ; goto S2
S2: XY := HL ; goto S3
S3: if ABC = XXL then XY := HL ; goto S3
  
```



- Are all input states covered? S0: LLX or HLX?
- Horizontal microcode
 - Each microinstruction is a "row" in the state table
 - State table is held in ROM, RAM or PLA
 - Input conditions encoded in addressing or selection
 - Often uses next μ address field (next state)
- Lexical analysis / parse table
 - Input is next character or symbol in scan
 - States / transitions to recognize composite constructs like numbers, identifiers, etc.
 - Instead of outputs, perform actions like store character, accumulate digit value, etc.

FSM types

 - Mealy machine
 - Named after G.H. Mealy
 - Outputs are function of present input and state



  
- Moore machine
 - Named after E.F. Moore
 - Output is strictly a function of machine state



Flip / flop per state

- Assign a flip / flop to each state
- Flip / flop is one when state is active (current)
- Sometimes called "one hot" sequential logic
- Need logic between state flip / flops

Inputs A B C	This state	Next state	Outputs X Y
LLX	S0	S1	LL
HHX	S0	S2	LH
XXX	S1	S2	LH
XXX	S2	S3	HL
XXL	S3	S3	HL
XXH	S3	S1	HH

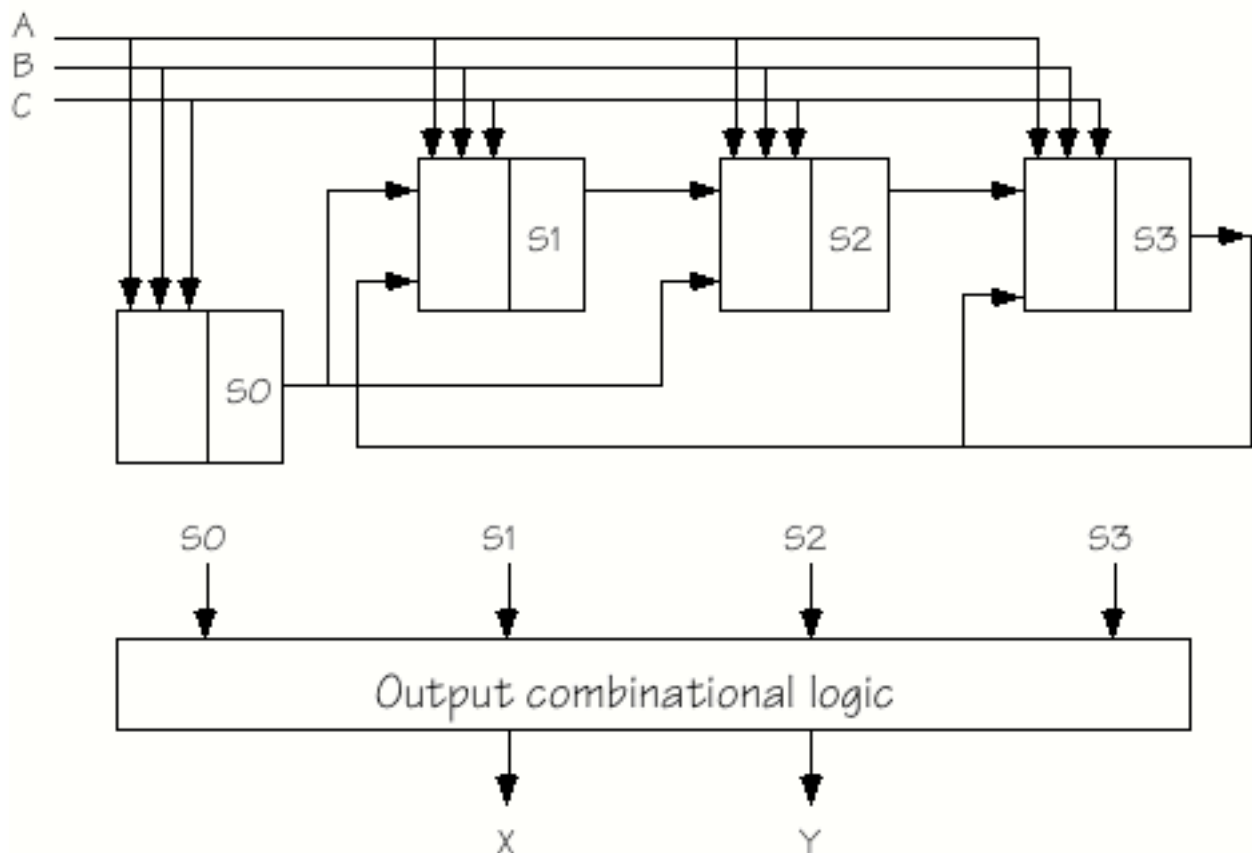

Encoded state

- Use an N-bit register to hold current state
- Assign each state a unique binary number
- Assume master - slave F/F operation

Inputs A B C	This state	Next state	Outputs X Y
LLX	S0	S1	LL
HHX	S0	S2	LH
XXH	S1	S2	LH
XXH	S2	S3	HL
XXL	S3	S3	HL
XXH	S3	S1	HH


Assign states

S0 → 0

S1 → 1

S2 → 2

S3 → 3

 

- Two master - slave flip / flops
 - Capture new state on rising edge
 - Change out to new state value on trailing edge
- Design problem centers on combinational logic
 - Five inputs: A, B, C, Q1, and Q0
 - Four outputs: X, Y, D1, and D0
 - Four sum of product equations (one per output)
 - Equations and logic could be minimized

Encoded state (2)

- Re-write state table with $D1$, $D0$, $Q1$ and $Q0$

Inputs A B C	This D1 D0	Next Q1 Q0	Outputs X Y
LLX	LL	LH	LL
HHX	LL	HL	LH
XXX	LH	HL	LH
XXX	HL	HH	HL
XXL	HH	HH	HL
XXH	HH	LH	HH

- Write sum of products equations $Q1$, $Q0$, X and Y


$$Q1 = A \cdot B \cdot \sim D1 \cdot \sim D0 + \sim D1 \cdot D0 + D1 \cdot \sim D0 + \sim C \cdot D1 \cdot D0$$

$$Q0 = \sim A \cdot \sim B \cdot \sim D1 \cdot \sim D0 + D1 \cdot \sim D0 + \sim C \cdot D1 \cdot D0 + C \cdot D1 \cdot D0$$

$$X = D1 \cdot \sim D0 + \sim C \cdot D1 \cdot D0 + C \cdot D1 \cdot D0 = D1$$



$$Y = A \cdot B \cdot \sim D1 \cdot \sim D0 + \sim D1 \cdot D0 + C \cdot D1 \cdot D0$$

 - Reduce and build gate network for each equation




Programmable logic arrays

- Often need to implement block of combinational logic
- Sum of products is really a two-level gate network
- Programmable logic array (PLA)
 - Two-level gate network
 - Provides a general framework for AND/OR logic
 - Separated into AND- and OR-planes
 - Framework forms true/complement of inputs
 - Program by adding transistors or connections
 - Add input and output latches to form FSM
- Advantages
 - Programmability, generation tools (CAD)
 - Regular, compact layout

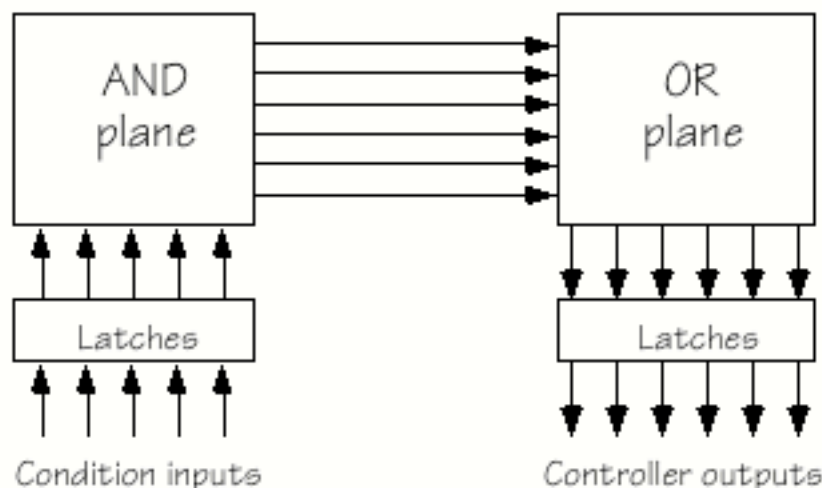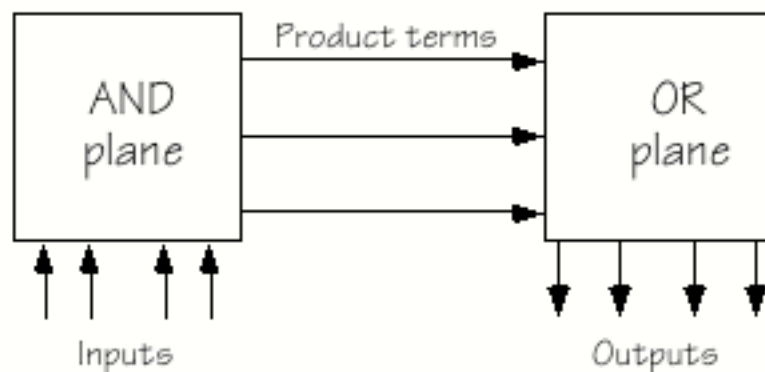

NOR-NOR PLA

 
- Typically use NOR-NOR logic
 - NAND array is slower
 - Long series chain of switches should be avoided
- Need to invert input terms (de Morgan's theorem)
- Not expensive as PLA's usually generate both true and complement forms of the inputs anyway




CMOS PLA implementations

- CMOS VLSI Design, Weste & Eshraghian, pg. 368
- Complementary gates complicate PLA layout
- Corresponding n- and p-gates must be connected
- Pseudo-nMOS
 - nMOS layout is simpler
 - Complementary gates not connected
 - Use p-channel device as pull-up resistor
 - Tie p-channel gate to ground; channel always ON
 - Requires ratio'd logic; choose L and W carefully
 - Static power consumption much higher
- Dynamic CMOS - 2-phase clocking
 - Latch inputs on Phi-1
 - Latch outputs on Phi-2
 - Precharge product term lines during \sim Phi-1
 - Set product term lines during Phi-1 (pull-down)
 - Approach #1
 - Generate internal OR-plane precharge clock
 - Must accommodate worst case loading delay
 - Self-timed logic
 - Precharge OR-plane when internal clock is low
 - Set output lines when internal clock asserted
 - Approach #2
 - Insert latch between AND and OR planes
 - Latch product terms on Phi-2
 - Latch OR-plane outputs on Phi-1
 - Pipeline register puts PLA one cycle behind
- Four-phase clocking
 - Extra intermediate latches
 - Must carefully apply timing discipline to design

Example AND-plane

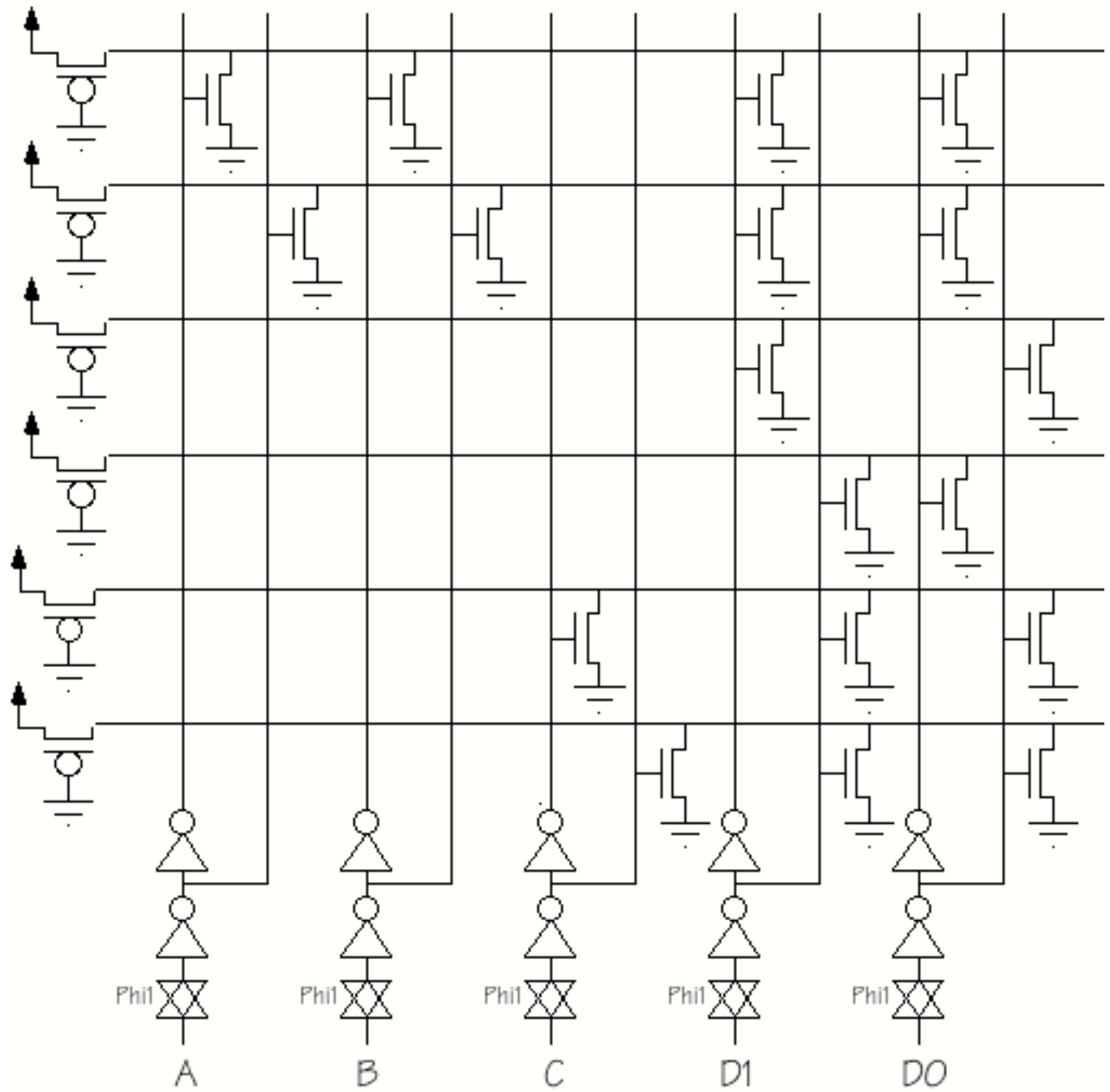


Example OR-plane

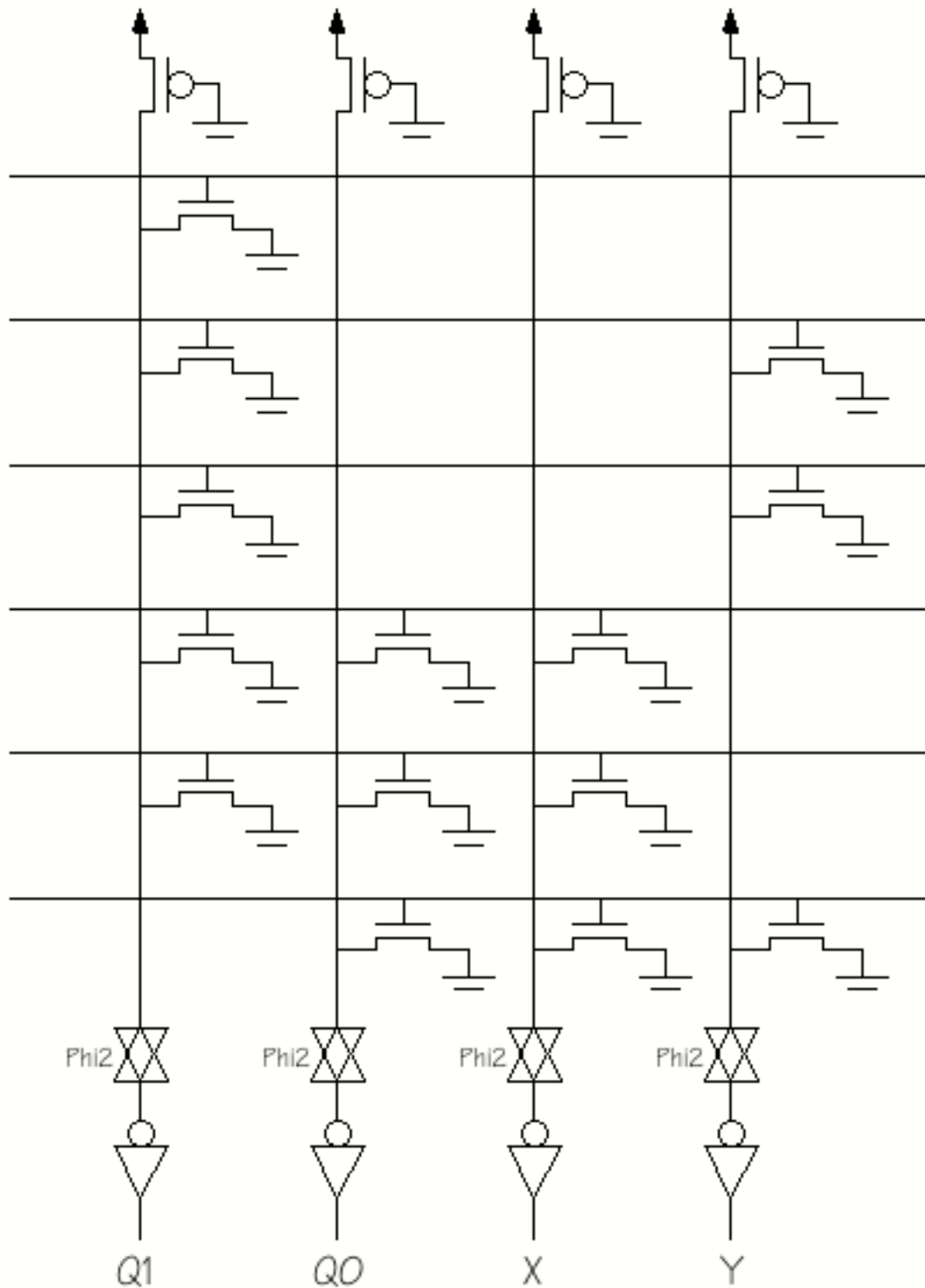


Microprogramming styles

- Horizontal microprogramming
 - Low degree of encoding
 - Apply microinstruction bits directly to control inputs
 - No encoding \Rightarrow less control delay
 - Results in very long microwords (32 to 300 bits!)
 - Exploitable parallelism
 - Theory to optimize microprogram size
- Vertical microprogramming
 - High degree of instruction encoding
 - Instructions resemble ordinary (ISA) programming
 - Microwords are short (16 to 32 bits)
 - Short microword \Rightarrow smaller control store
 - Typically cannot exploit as much parallelism
- Two-level control store (hybrid)
 - Take advantage of redundancy in control store
 - Short microinstruction indexes table of *nano* instructions
 - Nanoinstructions are unique *control states*
 - Apply nanoinstructions directly to control inputs
 - Example: Motorola 68000
 - ◊ Single level store: 52,400 bits
 - ◊ Two level store (total): 30,550 bits

 

Microinstruction design

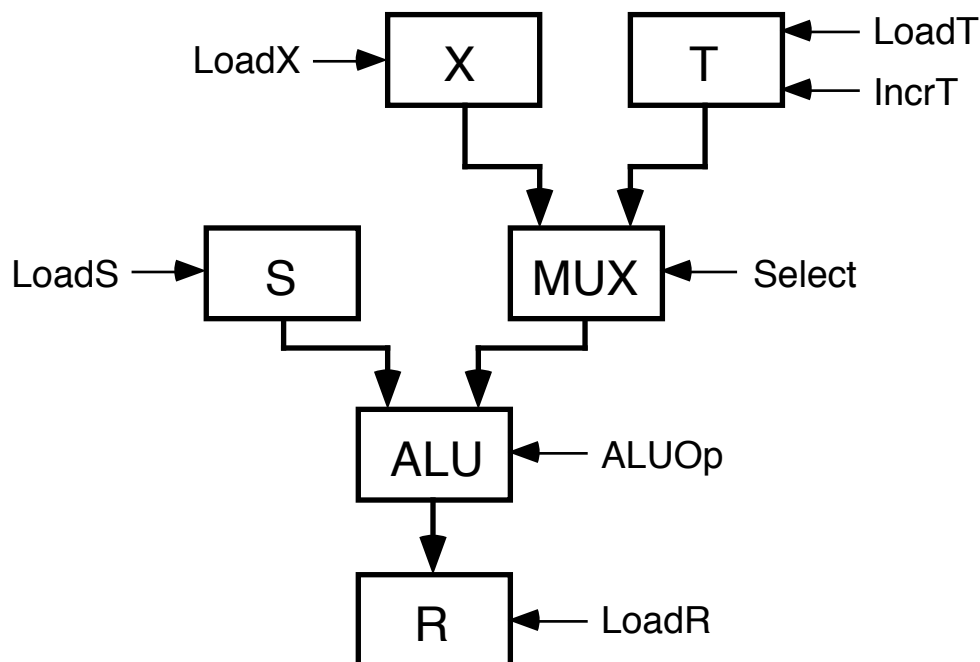- Make a list of all control signals in the datapath
 - ◊ Signal name(s)
 - ◊ Operation \leftrightarrow signal value table
- Add sequencing control signals
 - ◊ Next μ instruction address (branch address)
 - ◊ Branch condition selector
- Draw μ word format
 - ◊ Assign signals to μ instruction fields



LoadX
 0: No operation
 1: X \leftarrow new

value
 LoadS
 0: No operation
 1: S \leftarrow new

value
 LoadT
 0: No operation
 1: T \leftarrow new

value
 IncrT
 0: No operation

LoadR
 0: No operation
 1: R \leftarrow ALU

result
 ALUOp
 0: No operation
 1: Add
 2: Subtract
 3: AND
 4: etc.

Select
 0: Pass X
 1: Pass T


Microinstruction encoding

- Encode each graph block into one μ instruction
- Find datapath elements participating into transfers
- Select control signal values for each transfer

LoadX 0: No operation 1: $X \leftarrow$ new value	LoadR 0: No operation 1: $R \leftarrow$ ALU result
LoadS 0: No operation 1: $S \leftarrow$ new value	ALUOp 0: No operation 1: Add 2: Subtract 3: AND 4: etc.
LoadT 0: No operation 1: $T \leftarrow$ new value	Select 0: Pass X 1: Pass T
IncrT 0: No operation	

LoadX	LoadS	LoadT	IncrT	LoadR
0	0	0	0	1

ALUOp	Select	Branch
0 1	1	0 1 0

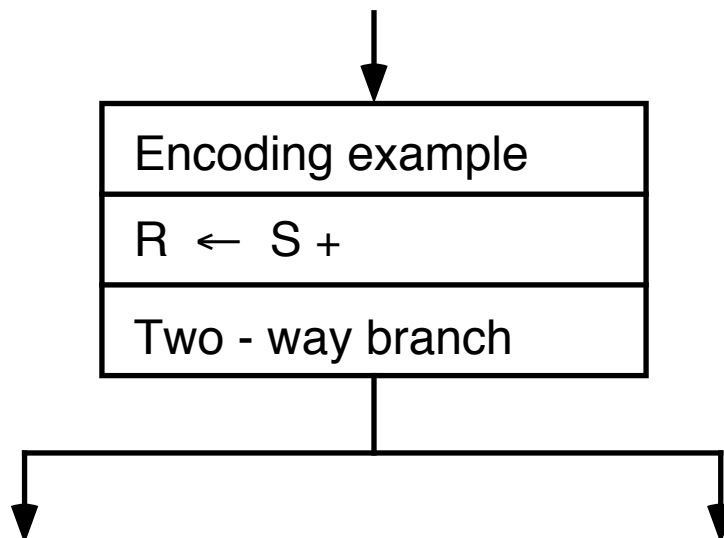


Levels of decoding


- ISA with multiple operation fields
- SP.3 example
 - Instruction tag field {stack, literal, op and desc call}
 - Multiple stack operations



- Two levels of decode

 


- One level of decode

 


- Move instruction
 - Most frequently executed instruction
 - Make instruction as fast as possible
 - Two level approach
 - Decode and identify move operation
 - Decode and identify addressing mode
 - Execute
 - One level approach
 - Decode and identify move absolute
 - Execute
 - Considerable savings will accrue

Overall design style

 - Central, synchronous control
- Two-phase, non-overlapping clock
- Separate control and datapath subsystems
 - Condition signals
 - ◊ Datapath state to be sensed
 - ◊ Controller will react to these values
 - ◊ List of values affecting control flow (sequencing)
 - Control signals
 - ◊ Evoke operations and transfers in the datapath
 - ◊ Effectively a list of all building block control inputs




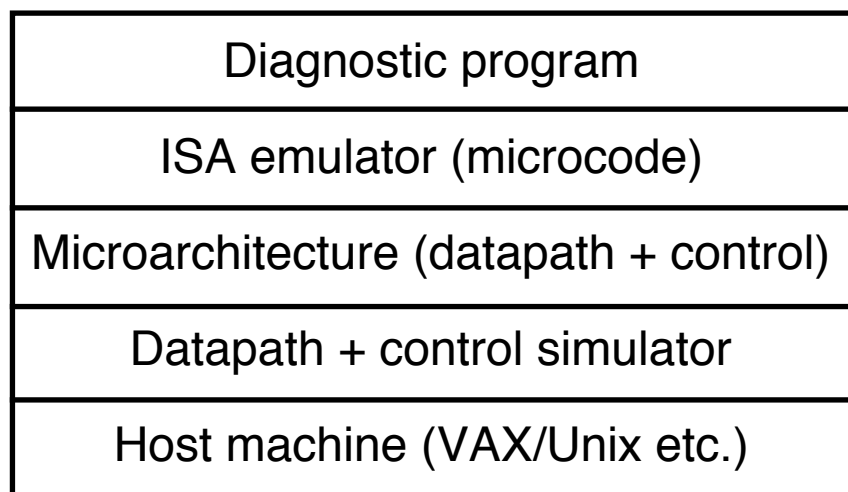- Microprogrammed control
 - Each control step is a microinstruction
 - A microinstruction is a bundle of control values
- Levels of virtual (abstract) machines




Programmable clock

 - Performance limited by slowest component
- Make clock speed selectable
- Choose the fastest speed possible for a transfer



- Two or more speeds

 


- Fixed speed versus programmable

Short operation R ← S	Fixed 195 nsec	Programmable 45 nsec
Long operation R ← S Δ	Fixed 195 nsec	Programmable 195 nsec


Pipelining

- Perform two or more operations concurrently
- Overlap two or more operations
- Usually later stages of pipe consume results of earlier stages

Instruction lookahead

 


Berkeley RISC machine

 

- Fetch: Get next instruction in sequence ($IP + 1$)
- Compute: Read dual port register file and compute result
- Store: Write result to destination register

SPARC pipeline

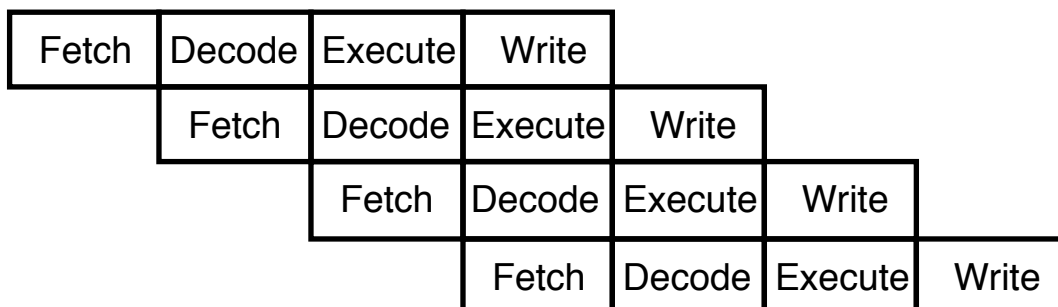

Pipeline problems

- Hazards
 - Data dependencies
 - Control dependencies
 - Collisions (resource conflict)
- Data dependency
 - Problem: Result is needed before it is stored
 - Example: Berkeley RISC
 - Solution: Detect hazard and forward result
- Control dependency
 - Problem: Branch occurs after prefetch
 - Example: Berkeley RISC and SPARC
 - Solutions
 - Flush and refill pipeline
 - Fill pipeline with no-op instructions
 - Delay the effect of the branch
 - ◇ Execute instructions already in pipe
 - ◇ Branch late
 - ◇ Compile code to use "extra" instruction effectively
 - ◇ Can successfully find work in 90% of the cases
- Collisions (resource conflicts)
 - Two instructions need the same resource
 - Detection and resolution
 - Static
 - ◇ Usually detect at decode stage
 - ◇ Conservative approach - hold until ready
 - Dynamic
 - ◇ Let instruction proceed
 - ◇ Detect and resolve at point of conflict
 - Usage counters
 - Scoreboarding