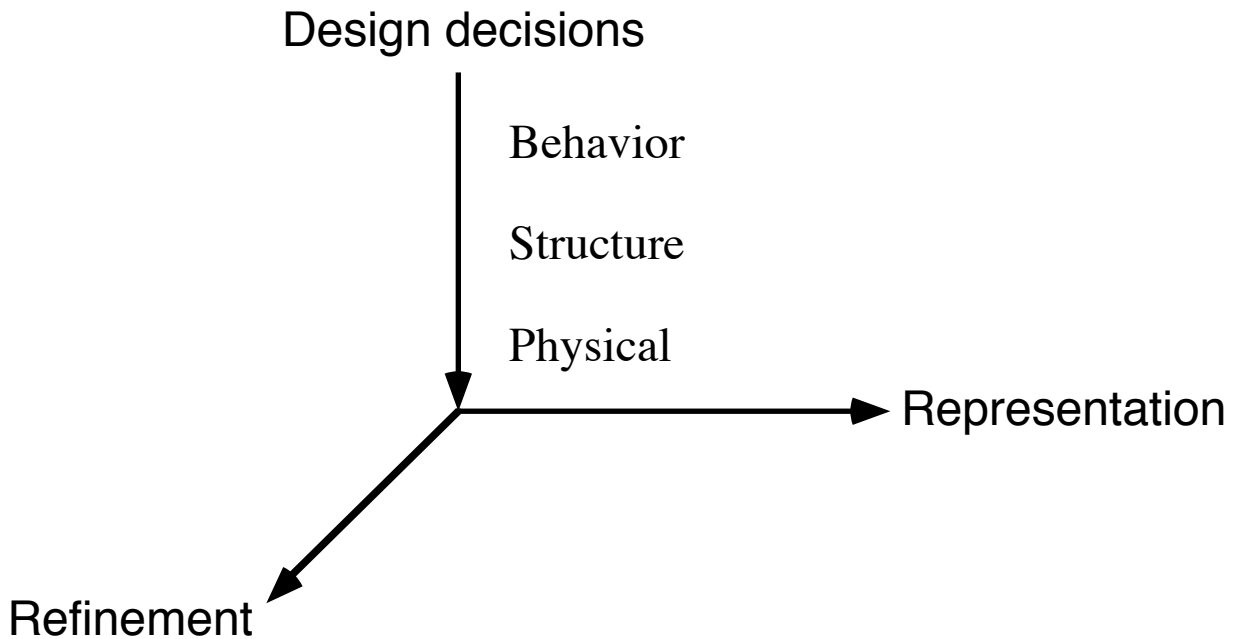


Computer design

Datapath synthesis and design style

P.J. Drongowski
SandSoftwareSound.net

Model of the design process




- Representation
 - Abstraction of design objects
 - Granularity
 - Large grain - design in the large
 - Small grain - detailed design
 - Levels
 - Architecture (abstract machine)
 - Organization (control plus datapath)
 - Logic / switch (gates and storage elements)
 - Electrical (electronic behavior)
 - Geometric (physical layout and properties)
- Design decisions
 - "Concurrent engineering" or "co-design"
 - Behavioral
 - Structural
 - Physical
- Refinement
 - Hierarchical design
 - Top-down decomposition into smaller subproblems
 - Bottom-up composition into larger subsystems

Design synthesis


- Transform specification to organization level design
 - Building blocks and connections
 - Control sequencing
- Satisfy engineering constraints and maintain correctness
 - Product characteristics
 - Speed
 - Space (packaging, appearance, etc.)
 - Current consumption (power supply size)
 - Power dissipation (packaging and cooling)
 - Reliability
 - Noise (immunity and radiation)
 - Technical feasibility
 - Market window versus project schedule
 - Price/performance point
 - Non-recurring engineering costs
 - Production costs
 - Promotion, marketing, advertising and administration
 - Profit
- Multidimensional problem
 - Determine datapath (building blocks and connections)
 - Define control and sequencing
 - Schedule computations for execution
 - Assign resources for computation
 - Adjust schedule and datapath for best mix

Overall design style

 - Central, synchronous control
- Two-phase, non-overlapping clock
- Separate control and datapath subsystems
 - Condition signals
 - ◊ Datapath state to be sensed
 - ◊ Controller will react to these values
 - ◊ List of values affecting control flow (sequencing)
 - Control signals
 - ◊ Evoke operations and transfers in the datapath
 - ◊ Effectively a list of all building block control inputs



 - Microprogrammed control
 - Each control step is a microinstruction
 - A microinstruction is a bundle of control values
- Levels of virtual (abstract) machines




Ad hoc synthesis technique

- Choose a bussing style
 - 0 bus: Data dependency driven connections
 - 2 bus: One read, one write bus
 - 3 bus: Two read, one write bus
- Translate C code into behavior graph
 - Use graph schemas for control constructs
 - Choose RT scheduling policy for initial cut
 - Maximally serial
 - Maximally parallel
 - Schedule and draw graphs for basic blocks
- Iteratively adjust datapath or control graph
 - More parallelism, additional components / busses
 - Select RT's to be merged into one control step
 - Is datapath adequate?
 - Add "private" operators or busses if necessary
 - Merge control steps
 - Fewer components / busses, more serial flow
 - Find control step to be split into two or more steps
 - Remove unneeded components or busses
 - Remove only if unneeded globally WRT control graph
- Adjust datapath delay, space and power mix
 - Faster delay path
 - Choose or design faster components
 - Collapse levels of multiplexing
 - Avoid or eliminate long busses
 - Decrease distance between critical components
 - Use less space
 - Try to remove components / busses from datapath
 - Select smaller components (possible speed penalty)
 - Dissipate less heat, lower current
 - Use efficient components on non-critical paths
 - Slow down critical path, increase parallelism

Behavior

- What is the behavior of the system?
- Organization level is sequencing plus register transfers
 - Sequencing represented in control graph
 - Register transfer
 - Parallel assignment statement
 - Transfer from sources to destinations via operators
 - Sources and destinations are registers, ports, memory
- Does the behavior execute fast enough?
 - Interacts heavily with structural and physical decisions
 - Increase parallelism with more components / busses
 - Combine or split control steps
 - Choose faster (higher power) components
 - Decrease (interconnect) bus lengths
 - Assign communicating subsystems to same chip


Control graph notation

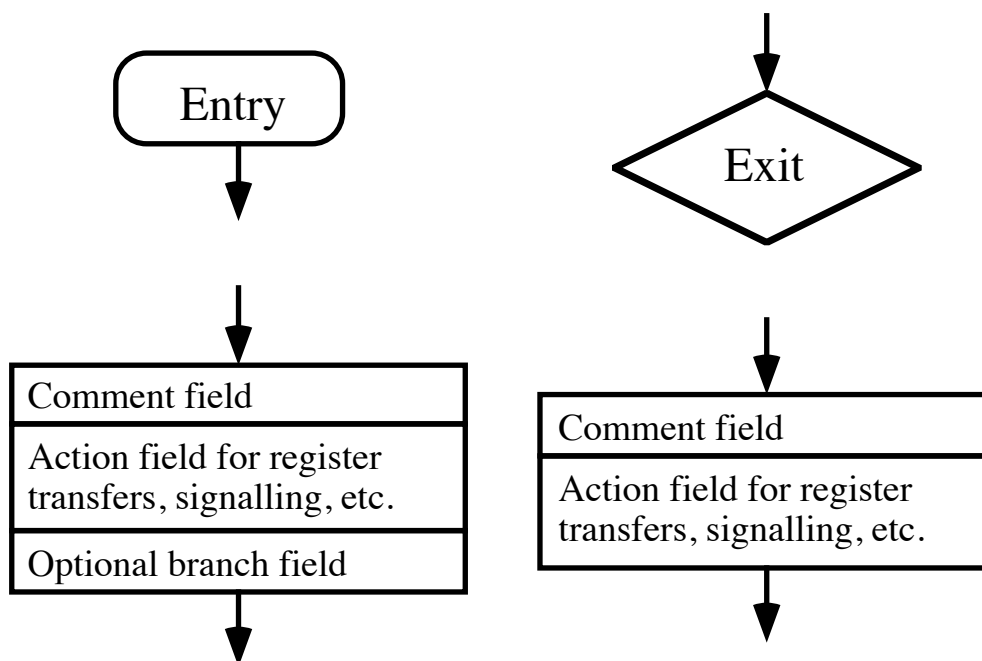

Control graph schemas


- Mapping from HLL control statement to graph
- Similar correspondence as source code to flowchart
 
```
if ( condition )  
  {  
    block-T  
  }  
else {  
  block-F  
}
```



- Conditions must be resolved into real signals
- Ok to have multi-way case branches
- Conditions can be AND'ed to decrease levels of branching

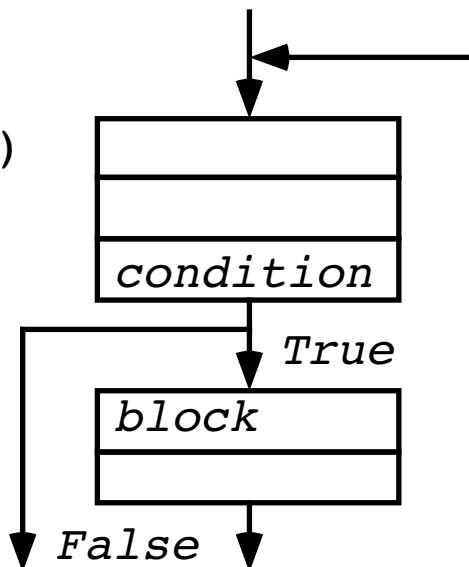
```
while ( condition )  
  {  
    block  
  }
```



Initial schedule


- Maximally serial
 - Assign each transfer to a single control step
 - Compatible with sequential, procedural HLL
 - Will have largest number of control steps
 - Fits well with 2- or 3-bus style
 - Steps may require splitting due to datapath restrictions

```
A = B + C ;  
IP = IP + 1 ;
```

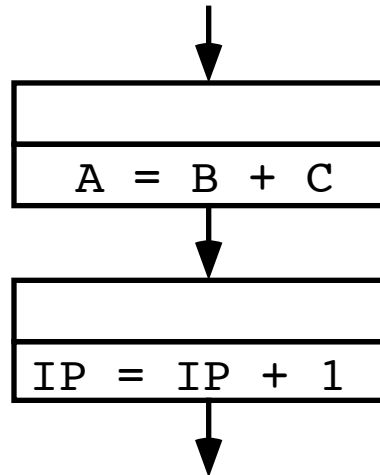

- Maximally parallel
 - Assign as many transfers to one step as possible
 - Transfer may be re-ordered if independent
 - Data dependency due to side-effect needs an extra step
 - Datapath may not have enough parallelism
 
```
A = B ;  
D = A + C ;  
IP = IP + 1 ;
```




- Could be combined to one step
- Action: $A = B ; D = B + C ; IP = IP + 1$

Structure


- What are the control, storage and operator resources?
- Structure is drawn in a block diagram
- How are the resources interconnected?
 - 0-bus style: Data dependency driven
 - 2-bus style: Read /write busses with common resources
 - 3-bus style: 2-read, 1-write bus with common resource
- How much space is consumed?
 - Delete component / bus \Rightarrow reschedule control graph
 - Reduce number of off-chip connections
 - Reduce power / speed \Rightarrow smaller size / drive transistors
- How much current is required (grid sizing?)
 - Reduce transistor size (drive) \Rightarrow lower transfer speed
 - High current \Rightarrow wide power distribution rails
- What is the power dissipation (cooling?)
 - Reduce current / speed of non-critical paths
 - Decrease number of off-chip connections (esp. outputs)
- Control
 - Must provide control component (FSM, etc.)
 - Establish interconnection for:
 - Datapath conditions to controller
 - Control signals from controller to datapath
 - Translate control graph to control "programming"

Bus styles

 
- 0 bus - data dependency driven design
 - Will probably yield the most parallelism
 - Some parallelism may go unused or be too costly
 - Build list of all data dependencies
 - Allocate operator or bus as needed
 - Example abstract transfer: $C \leftarrow A + B$



 - 2 bus - one read, one write bus
 - Highly sequential RT scheduling
 - Conservative use of busses; easy to layout
 - Need temporary register for dyadic operations




 - 3 bus - two read, one write bus
 - One step evaluation of dyadic operation
 - Good fit with dual port register file, ALU




Busses

 - Bus split (or rip)
 - Selectively route wires from source to destination
 - What is the datatype of the result? Unsigned?
 - Example: $R = X\langle 7:4 \rangle$; $S = X\langle 3:0 \rangle$



- Bus join (or concatenate)
 - Route wires to different bits of common destination
 - Assign transfers to same machine step if possible
- Source and destination of different word sizes (length)
 - Assume R is N bits, S is M bits
 - $N > M$: $R = S$;
 - Assign S to $R\langle M-1:0 \rangle$
 - Set $R\langle N:M \rangle$ to 0?
 - Leave $R\langle N:M \rangle$ unaffected?
 - $N < M$: $R = S$;
 - Assign $S\langle N-1:0 \rangle$ to R
 - Bits $S\langle M:N \rangle$ are discarded (unconnected)
 - May need to clock portions of register independently

 

Variables


- Kinds of variables
 - Communication ports
 - Data ports (in, out, bidirectional)
 - Control ports (signalling, synchronization)
 - Architectural registers or memory
 - Part of the visible interface or ISA
 - Must be included in design
 - Temporary registers or memory
 - Hidden storage
 - Can be flexibly scheduled (shared)
- Implementation styles
 - Dedicated register
 - Can add intrinsic operations
 - More exploitable datapath parallelism
 - Register file (scratchpad RAM)
 - No special intrinsic operations
 - Sequential access to variables
 - Large, read / write memory
 - Can hold a large number of variables
 - Usually requires off-chip memory subsystem
- Live variable analysis
 - Determine variable lifetime
 - Construct register compatibility graph
 - Find set of disjoint registers for each register
 - Edge represents disjoint usage times of 2 registers
 - Merge registers with disjoint lifetimes
 - Good especially for temporary registers
 - Algorithms
 - Clique partitioning (NP-complete)
 - Graph coloring

Register transfers

- Each RT has implications for:
 - ◊ Binding of variables to storage or ports
 - ◊ Selection of and binding to operator components
 - ◊ Interconnection and possibly multiplexing
 - ◊ Routing of data through the datapath
- Scheduling of RT's can affect:
 - ◊ Variable and operator bindings
 - ◊ Availability of routes through datapath
- Heuristics
 - Serial execution permits more sharing
 - Parallel execution needs more dedicated resources
 - Parallel execution may cause resource conflicts


Simple register transfer

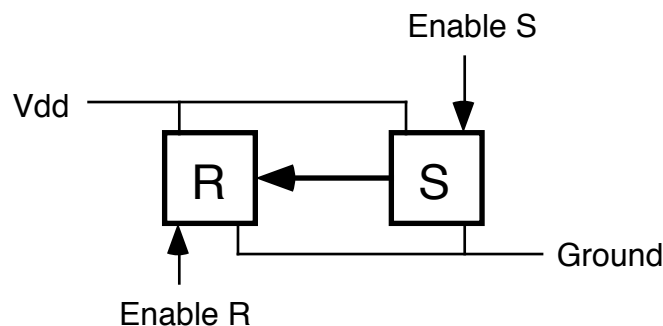- Transfer from one register to another: $R = S ;$
- Implications
 - Two storage objects for S and R
 - A path from S to R
 - Connect LSB's to LSB's: $R\langle N:0 \rangle = S\langle M:0 \rangle ;$
 - Enable (control) signals routed to controller
 - Power connections must be made to rails
- Dead variable analysis for temporary binding to register




Complex register transfers

 - Register indices must be computed
- Choices
 - Produce index from controller (μ word)
 - Generate with dedicated hardware
 - Route from register field (e.g., IP)
 - Compute with shared hardware
- Example: $R[i] = S[j]$;
- R and S must be register files (scratchpad)





- Function call on right hand side (RHS)
- Does the function have side-effects?
 - Yes
 - Implies a parallel control (execution) flow, or
 - A serial "subroutine" to be called / expanded in-line
 - Must be scheduled WRT control graph
 - Difficult problem; disallow side-effects
 - No
 - Can be implemented as combinational logic
 - Decompose function into library components
 - Generate PLA for logic function
- Example: $R = f(A, B)$;

 


General registers

- Register to register architecture
$$R[i] \leftarrow R[j] \Delta R[k]$$
- Single port RAM implementation
 - Only one value can be read at a time
 - Sequential computation needed
$$X \leftarrow R[j]$$
$$Y \leftarrow Y \Delta R[k]$$
$$R[i] \leftarrow Y$$
- Dual port RAM implementation
 - Two read ports; two values out at a time
 - Reduce to two step evaluation
$$Y \leftarrow R[j] \Delta R[k]$$
$$R[i] \leftarrow Y$$

  


Constants

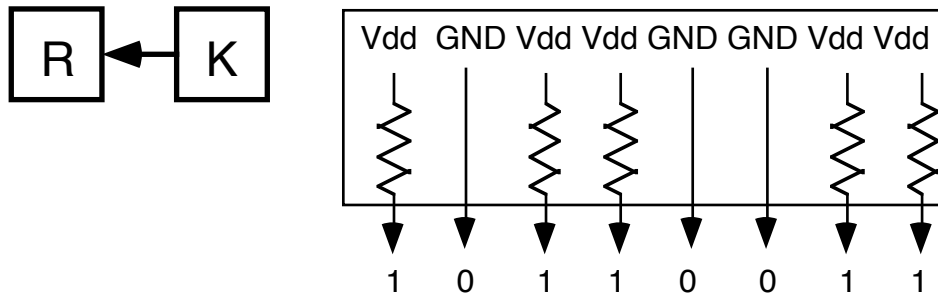
- Constants must be stored somewhere!
- Single constant
 - Connect outputs to Vdd or ground
 - Use current limiting resistors



 - Read only memory (ROM) implementation
 - Useful if several constants are needed
 - Generate index from controller (μ word) or datapath




 - Microinstruction "emit field"
 - Control program is often stored in ROM
 - Design field into microword to emit constant
 - Bits are allocated even if unused (disadvantage)
 - Access to only one constant at a time



External input / output

- Chip must be connected to printed circuit board
 - Die is mounted in a carrier package
 - Carrier has traces leading to pins
 - Pins connect to PCB-level pads and wires
 - Wires must be bonded to chip and carrier traces
 - Chip connections are made to metal "bonding pads"
 - Pads must be placed at perimeter of die
- Typical component sizes ($1\ \mu\text{m} = 1\ \text{micron}$)
 - Transistor: $1\ \mu\text{m} \times 1\ \mu\text{m}$
 - Metal wire: $3\ \mu\text{m}$ wide
 - Bonding pad: $100\ \mu\text{m} \times 100\ \mu\text{m}$
 - Human hair: $40\ \mu\text{m}$ diameter
- Input
 - Voltage level shifting or hysteresis
 - Static protection
- Output
 - Must drive large off-chip wires ($10+$ pF capacitance)
 - Drive transistor: $80\ \mu\text{m} \times 1\ \mu\text{m}$
 - Large current requirement and power dissipation
- Bidirectional
 - Permits bidirectional flow of data
 - Must have a disconnected (high-Z) state
- Power supply (e.g., V_{dd} and ground)

 


Dedicated versus general

- Trade-off is not simple or obvious
- Consider the example below


$$R = S + T ;$$

$$R = S - T ;$$

- + and - could be bound to an

 

 - Or, two dedicated operators could be allocated
- Note extra delay due to multiplexing
- Routing complexity is potentially higher, too



- Which solution requires less area?
- Dissipates less heat?
- How do wire lengths affect delay?


Data operations

- Intrinsic operations
 - Operations that can be performed in place
 - Avoid additional combinational logic and wiring
 - Choose library component with operations built-in
 - Shift and count not usually implemented together
 - Must add extra control lines


Transfer	Name	Component
$R = 0$	Clear	Register
$R = 0xF \bullet \bullet F$	Preset	Register
$R = R + 1$	Increment	Counter
$R = R - 1$	Decrement	Counter
$R = R / 2$	Shift right	Shift register
$R = R * 2$	Shift left	Shift register

- Dedicated operator component
 - Map operator directly to combinational component
 - Should yield most parallelism
 - Costly in space, current, power, interconnect
 - Many stages of logic will slow clock speed
 - ◊ Longer, fewer steps versus
 - ◊ More steps of shorter duration
 - Exploit commutivity where ever possible
 - Non-commutative operators constrain interconnection
- "Generalized" operator component
 - Typical example is an arithmetic logic unit (ALU)
 - Good choice in serial flow with opportunity for sharing
 - May force long wires to be routed to central resource
 - ◊ Wire delay could dominate switching delay
 - ◊ Selectively employ dedicated components
 - See comments on commutivity above

Left and right shift

 


Byte swap

 


Barrel switch

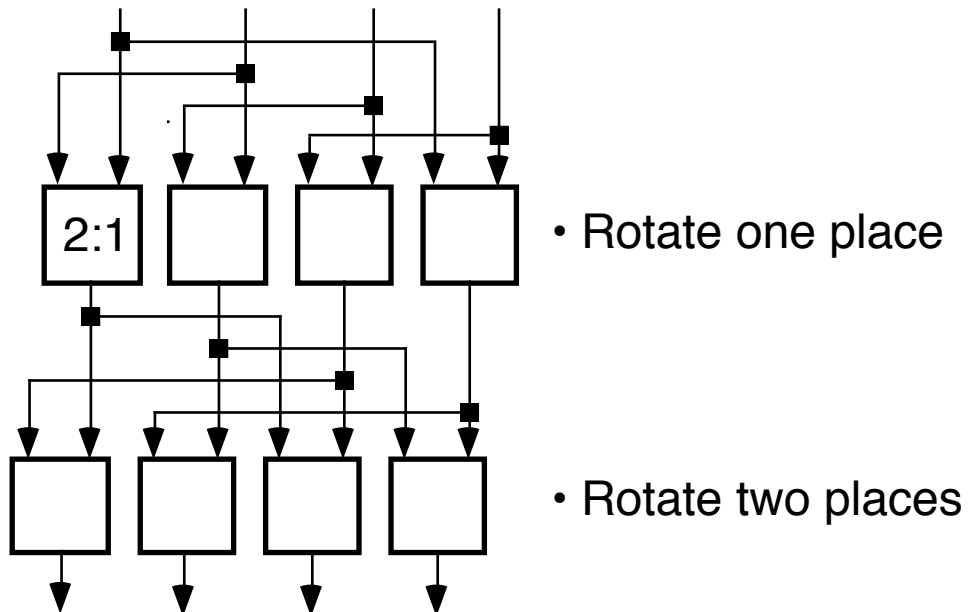- Rotate multiple places left or right
- Mask to obtain shifted data




Why wait?

- Common three bus structure

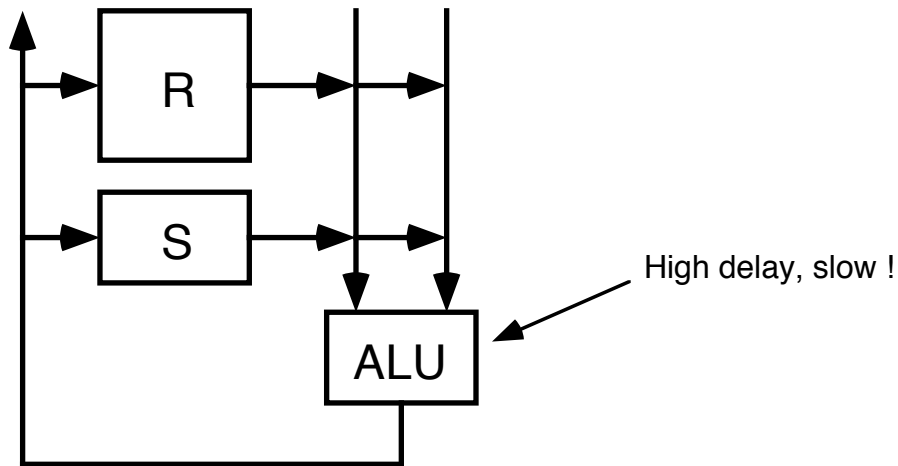

 
- Bottleneck
 - ALU adds delay to simple transfers: $S \leftarrow R$




- But! Clock period is determined by slowest component.
- Make clock rate variable instead.

Programmable clock

 - Performance limited by slowest component
- Make clock speed selectable
- Choose the fastest speed possible for a transfer



- Two or more speeds

 

- Fixed speed versus programmable

Short operation R ← S	Fixed 195 nsec	Programmable 45 nsec
Long operation R ← S Δ	Fixed 195 nsec	Programmable 195 nsec

Physical

- Where should components be placed?
- Size and arrangement are shown in floor plan
- Increase speed of critical register transfer
 - Move components on path closer
 - Add private bus instead of using long bus
 - Increase drive (power) on critical path
- Reduce component area
 - Eliminate component \Rightarrow reschedule control graph
 - Use smaller drive transistors \Rightarrow slower transfers
- Reduce interconnect area
 - Use wiring by abutment and pitch matching
 - Move components closer together (compact layout)
- Decrease size of power grid
 - Decrease current requirements of subsystems
 - Do not exceed maximum current density of wires
- Reduce off-chip connections
 - Bonding pads are 10,000 times as big as transistors
 - Outputs are chief source of heat (roughly 40 percent)
- Other concerns
 - Noise
 - Quality of the power supplied
 - Clocks, power and control must be routed globally
 - Few layers for wire routing