

VLSI design

Introduction to CMOS circuits

P.J. Drongowski
SandSoftwareSound.net

Digital circuit technology


- Representation
 - Decision and computation
 - Storage (memory)
 - Energy loss
-

Binary representation

- Absence/presence of charge
- Example
 - Absence = "0" (0 Volts)
 - Presence = "1" (+5 Volts)


Decision and computation

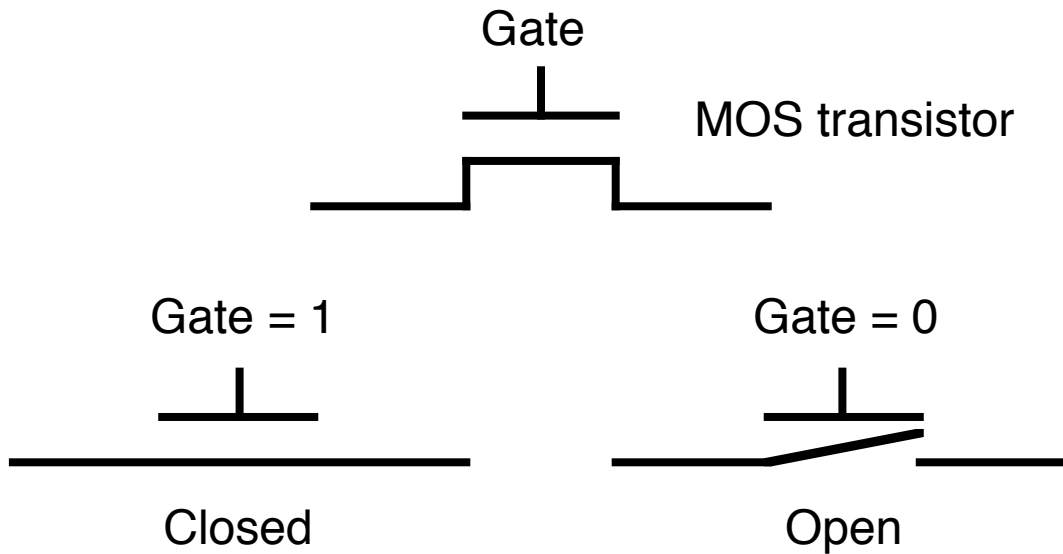- Charge (voltage) controlled switch
- Example: MOS transistor switch




Information storage

 - Capacitor (charge storage)
- Example: MOS transistor




Energy loss

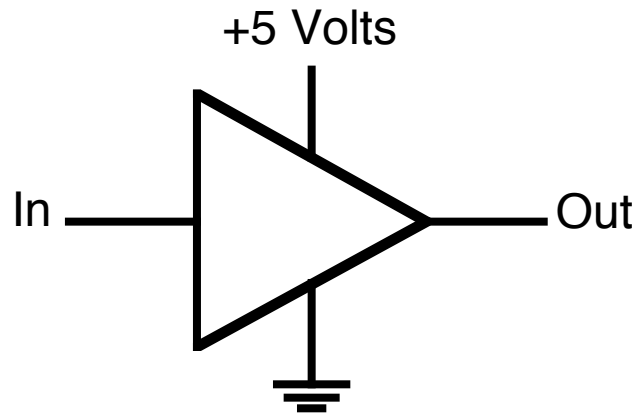
- Restoring logic
- Amplification
- Power supply




Simplified transistor structure

 


V_{gs} vs. I_{ds}

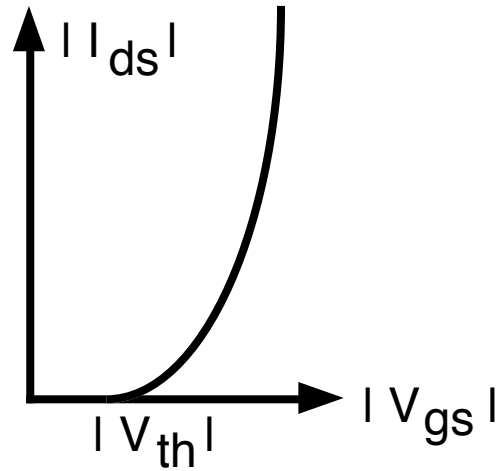


V_{ds} vs. I_{ds}

 

CMOS inverter

 


CMOS logic gates

 

Choosing transistor sizes (W and L)

- Delay
 - Rise time
 - Fall time
- Current consumption
- Power dissipation


Channel width and length

 

Rise time

- Time to rise from 10% to 90% of final value.
- Pull-down transistor is off.
- Pull-up channel and load form an RC circuit.
 
$$T_{rise} = 4 \frac{C_{load}}{\beta \times V_{dd}} \quad \beta = \frac{\mu \times \epsilon}{T_{ox}} \frac{W}{L}$$



$$\epsilon = 35 * 10^{-14} \text{ F / cm}$$

Permittivity of gate oxide

$$\mu = 1000 \text{ cm}^2 / \text{V-sec}$$

Hole surface mobility


$$T_{ox} = 5 \text{ microns}$$

Thickness of gate oxide

Fall time

- Time to fall from 90% to 10% of final value.
- Pull-up transistor is off.
- Pull-down channel and load form an RC circuit.
 
$$T_{\text{fall}} = 4 \frac{C_{\text{load}}}{\beta \times V_{\text{dd}}} \quad \beta = \frac{\mu \times \epsilon}{T_{\text{ox}}} \frac{W}{L}$$



$$\epsilon = 35 * 10^{-14} \text{ F / cm}$$

Permittivity of gate oxide

$$\mu = 500 \text{ cm}^2 / \text{V-sec}$$

Electron surface mobility


$$T_{\text{ox}} = 5 \text{ microns}$$

Thickness of gate oxide

Effect of dissimilar beta values

- $\beta_n = 2 \times \beta_p$
 - Then, $T_{fall} = \frac{T_{rise}}{2}$
 - For symmetric rise and fall, $\frac{\beta_n}{\beta_p} = 1$
 - Therefore, $W_p = 2 \times W_n$
-

Effect on DC transfer characteristics

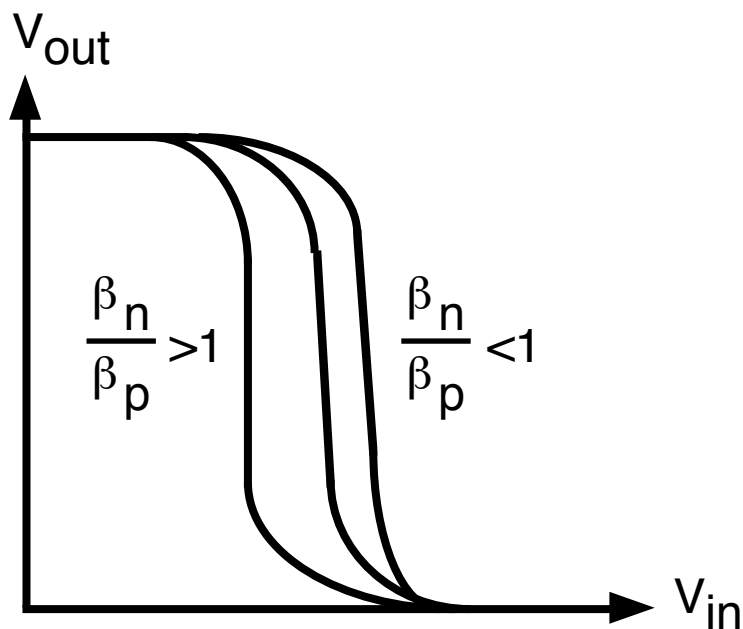

Static power dissipation

$$P_s = \sum_1^n \text{leakage current} \times \text{supply voltage}$$

- n is the number of devices
- Supply voltage is typically +5 Volts
- Leakage current is 0.1nA to 0.5nA per gate (25° C)
- Lower supply voltage \Rightarrow lower dissipation!

Dynamic power dissipation

$$P_d = C_{\text{load}} \times V_{\text{dd}}^2 \times f$$


- During transitions (0 \Rightarrow 1, 1 \Rightarrow 0), both transistors are ON
- Short current pulse from Vdd to ground
- Current is required to (dis)charge load capacitance

Total power dissipation


$$P_{\text{total}} = P_s + P_d$$

- Portions of design may operate at different frequencies

CMOS transmission gate

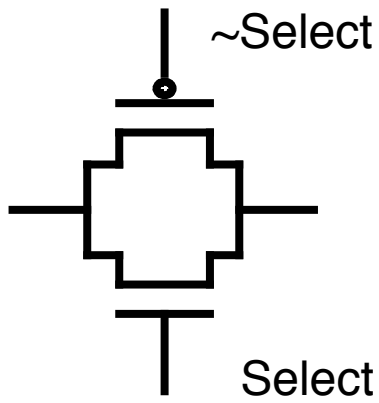


Normally open

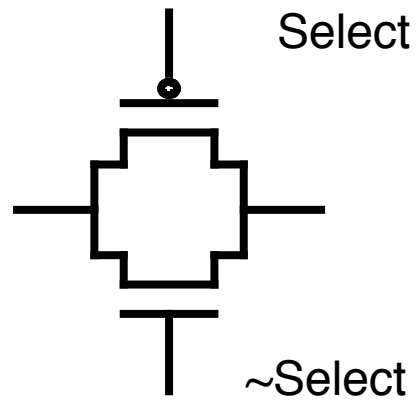


Normally closed


CMOS multiplexer

 


CMOS dynamic D latch

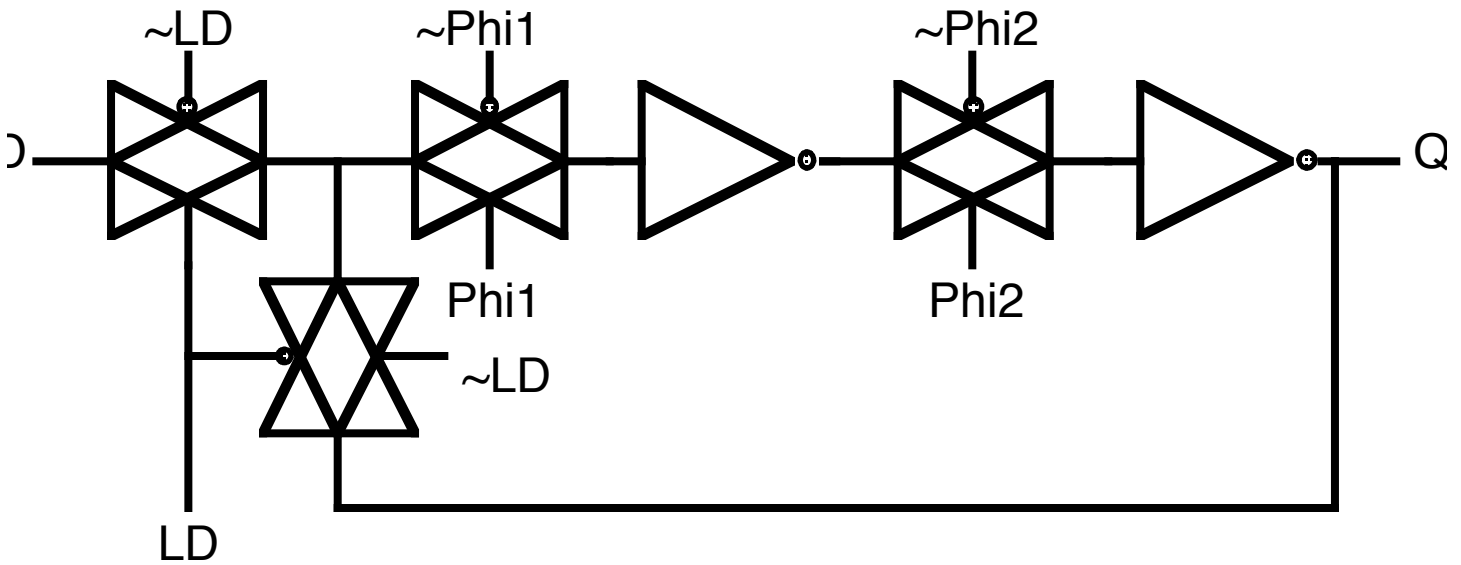


CMOS static D latch

 


Static CMOS RAM

 

Dual port RAM

 

CMOS content addressable memory

 


- Write operation
 - Place D and $\sim D$ on data lines
 - Assert the select line S
- Read operation
 - Precharge D and $\sim D$ lines
 - Assert select lines
 - Either D or $\sim D$ will be pulled down
- Compare operation
 - Precharge match line
 - Put pattern data on $\sim D$
 - Put complement of data on D
 - If data matches, pull-down will remain OFF
 - If data does not match, match line is pulled down

Binary full-adder

A	B	C	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


NAND and XOR implementation

 


Domino logic

- Clocked CMOS combinational logic
- Add CMOS buffer to output of each logic stage
- Precharge dynamic gate high ($\Phi = 0$)
- Conditionally discharge during evaluate ($\Phi = 1$)
- Dynamic gate can only transition from 1 to 0
- Output of buffer only transitions from 0 to 1
- Cascaded logic evaluates and "falls" in turn
- Limitations
 - Only non-inverting logic is possible
 - Each gate must be buffered
 - Charge distribution in large structures

CMOS domino sum

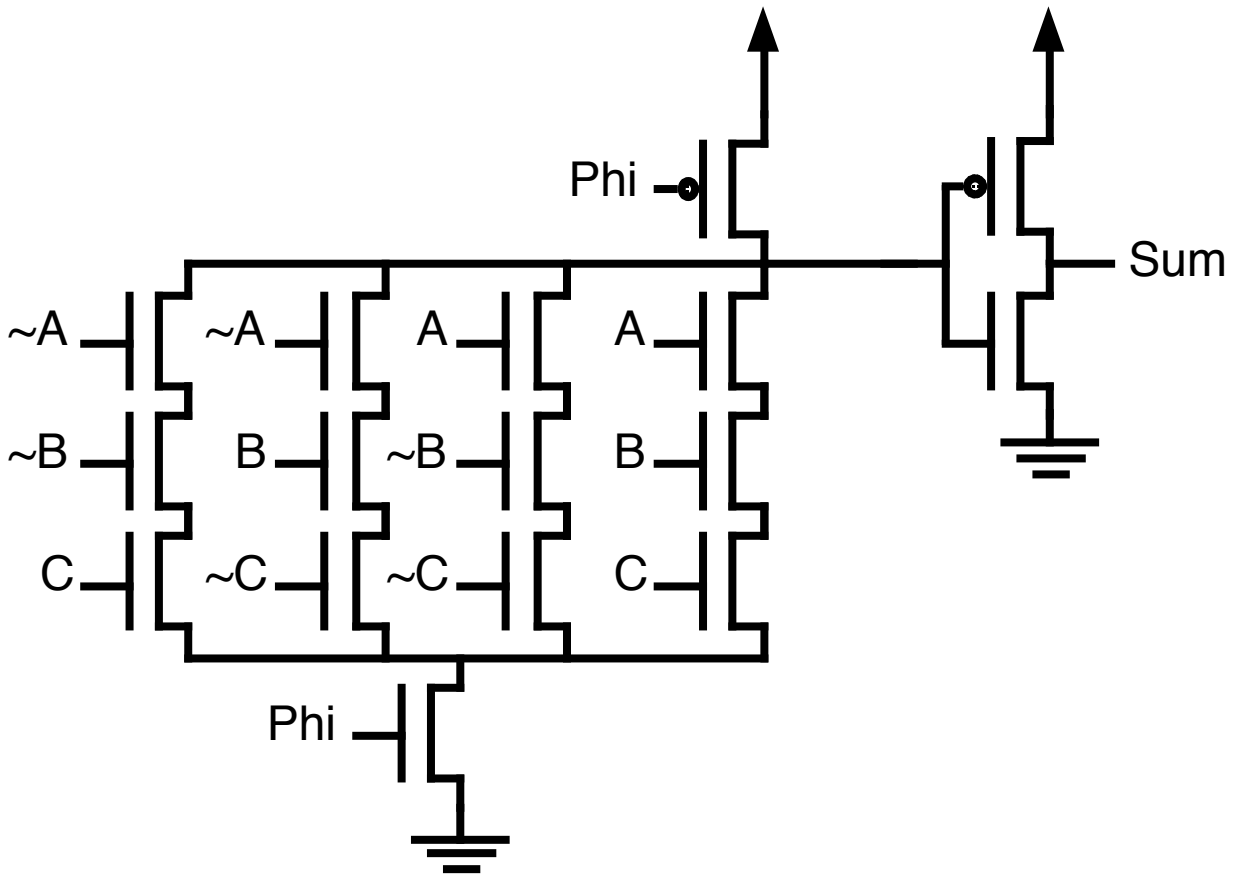

Compare

 

Material

- Capacitance ($\lambda = 1.5 \mu\text{m}$)
 - Unit is capacitance per square micron of area
 - Compute area and multiply by material constant

Gate	4.5×10^{-4}		
Polysilicon over field	0.5×10^{-4}		
n-diffusion (active)	0.9×10^{-4}	pF /	2
p-diffusion (active)	0.9×10^{-4}		
Metal 1 over field	0.2×10^{-4}	μm	
Metal 2 over field	0.1×10^{-4}		

- Resistance
 - Sheet resistance
 - Count number of squares of material
 - Multiply by material constant

- Resistance $R = \frac{\rho}{t} \frac{L}{W}$

ρ = Resistivity


t = Thickness

L = Conductor length

W = Conductor width

Metal	0.5 Ohms / square
Silicides	3 Ohms / square
Diffusion	25 Ohms / square
Polysilicon	50 Ohms / square

Growth of complexity

 

Processor	Transistors
4004	2,300
8080	6,000
8086	29,000
80286	134,000
80386	275,000
i860	1,000,000
i486	1,200,000

Microcomputer Solutions, Intel Corporation, 1989.