
 


Ripple-carry adder

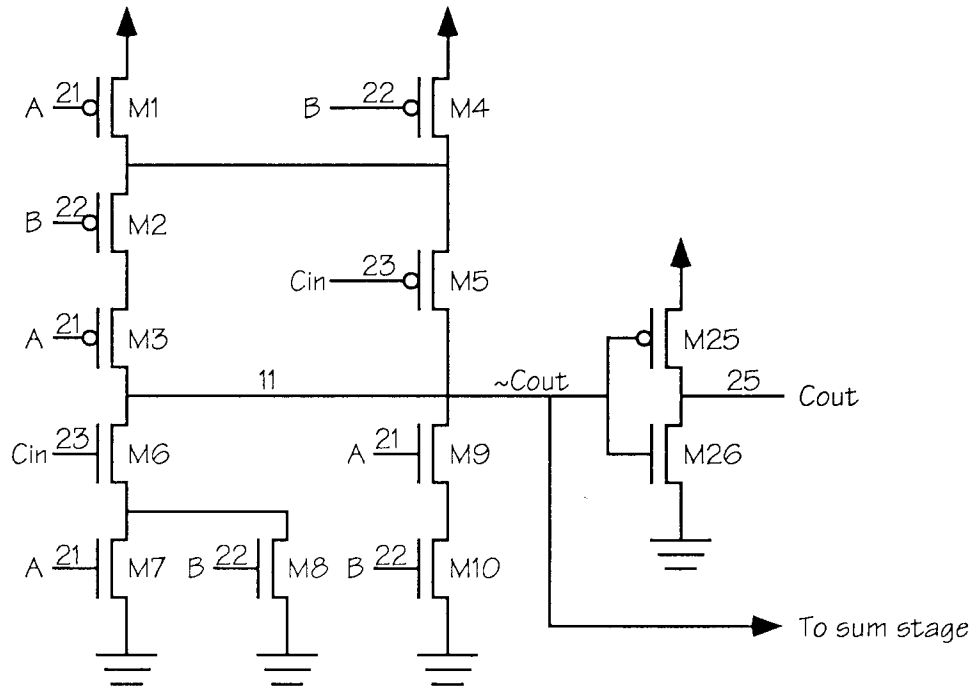

1 February 1991

Spice example: Full adder

```
.SUBCKT FADDER 21 22 23 24 25 26
* Full adder - I/O node assignments
*   A      21
*   B      22
*   Cin    23
*   Sum    24
*   Cout   25
*   +5V    26
* Internal node numbers: 1:10
*   CBar = 11
*   SBar = 12

* Mx ND NG NS NB mname L=val W=val
M1  10 21 26 26 CMOSP L=2U W=4U
M2   1 22 10 26 CMOSP L=2U W=4U
M3  11 21  1 26 CMOSP L=2U W=4U
M4  10 22 26 26 CMOSP L=2U W=4U
M5  11 23 10 26 CMOSP L=2U W=4U
M6   2 23 11  0 CMOSN L=2U W=2U
M7   2 21  0  0 CMOSN L=2U W=2U
M8   2 22  0  0 CMOSN L=2U W=2U
M9   3 21 11  0 CMOSN L=2U W=2U
M10  3 22  0  0 CMOSN L=2U W=2U
M11  4 23 26 26 CMOSP L=2U W=4U
M12  4 21 26 26 CMOSP L=2U W=4U
M13  4 22 26 26 CMOSP L=2U W=4U
M14 12 11  4 26 CMOSP L=2U W=4U
M15  5 21  4 26 CMOSP L=2U W=4U
M16  6 22  5 26 CMOSP L=2U W=4U
M17 12 23  6 26 CMOSP L=2U W=4U
M18  7 11 12  0 CMOSN L=2U W=2U
M19  7 21  0  0 CMOSN L=2U W=2U
M20  7 22  0  0 CMOSN L=2U W=2U
M21  7 23  0  0 CMOSN L=2U W=2U
M22 12 23  8  0 CMOSN L=2U W=2U
M23  8 21  9  0 CMOSN L=2U W=2U
M24  9 22  0  0 CMOSN L=2U W=2U
* Invert to get Cout
M25 25 11 26 26 CMOSP L=2U W=4U
M26 25 11  0  0 CMOSN L=2U W=2U
* Invert to get Sum
M27 24 12 26 26 CMOSP L=2U W=4U
M28 24 12  0  0 CMOSN L=2U W=2U
.ENDS
```

Subcircuit name and I/O nodes

Comments

Minimum size transistors

Spice example: 16 bit ripple carry adder

* Node assignments

*

* A<15:0> - 16 to 1

* B<15:0> - 36 to 21

* Cin - 40

* Cout<15:0> - 56 to 41

* Sum<15:0> - 76 to 61

*	A	B	Cin	Sum	Cout	Vdd	
XADD0	1	21	40	61	41	100	FADDER
XADD1	2	22	41	62	42	100	FADDER
XADD2	3	23	42	63	43	100	FADDER
XADD3	4	24	43	64	44	100	FADDER
XADD4	5	25	44	65	45	100	FADDER
XADD5	6	26	45	66	46	100	FADDER
XADD6	7	27	46	67	47	100	FADDER
XADD7	8	28	47	68	48	100	FADDER
XADD8	9	29	48	69	49	100	FADDER
XADD9	10	30	49	70	50	100	FADDER
XADDA	11	31	50	71	51	100	FADDER
XADDB	12	32	51	72	52	100	FADDER
XADDC	13	33	52	73	53	100	FADDER
XADDD	14	34	53	74	54	100	FADDER
XADDE	15	35	54	75	55	100	FADDER
XADDF	16	36	55	76	56	100	FADDER

16 full adders

Instance name

Subcircuit name

16 bit ripple carry adder: Input voltage sources

* Inputs to full adder

Piecewise linear voltage source
+ node / - node
Time - voltage pairs

```


VA0 1 0 PWL 0N 0V 160N 0V
VA1 2 0 PWL 0N 0V 160N 0V
VA2 3 0 PWL 0N 0V 160N 0V
VA3 4 0 PWL 0N 0V 160N 0V
VA4 5 0 PWL 0N 0V 160N 0V
VA5 6 0 PWL 0N 0V 160N 0V
VA6 7 0 PWL 0N 0V 160N 0V
VA7 8 0 PWL 0N 0V 160N 0V
VA8 9 0 PWL 0N 0V 160N 0V
VA9 10 0 PWL 0N 0V 160N 0V
VAA 11 0 PWL 0N 0V 160N 0V
VAB 12 0 PWL 0N 0V 160N 0V
VAC 13 0 PWL 0N 0V 160N 0V
VAD 14 0 PWL 0N 0V 160N 0V
VAE 15 0 PWL 0N 0V 160N 0V
VAF 16 0 PWL 0N 0V 160N 0V
VB0 21 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB1 22 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB2 23 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB3 24 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB4 25 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB5 26 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB6 27 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB7 28 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB8 29 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VB9 30 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBA 31 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBB 32 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBC 33 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBD 34 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBE 35 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VBF 36 0 PWL 0N 0V 40N 0V 50N 5V 160N 5V
VCin 40 0 PWL 0N 0V 80N 0V 90N 5V 120N 5V
+ 130N 0V 160N 0V
    
```

16 bit ripple carry adder: Loads and analysis

* Capacitive load on adder outputs


```
CS0 61 0 0.01P
CS1 62 0 0.01P
CS2 63 0 0.01P
CS3 64 0 0.01P
CS4 65 0 0.01P
CS5 66 0 0.01P
CS6 67 0 0.01P
CS7 68 0 0.01P
CS8 69 0 0.01P
CS9 70 0 0.01P
CSA 71 0 0.01P
CSB 72 0 0.01P
CSC 73 0 0.01P
CSD 74 0 0.01P
CSE 75 0 0.01P
CSF 76 0 0.01P
```

Capacitor name
+ node / - node
Capacitance



```
CC0 41 0 0.01P
CC1 42 0 0.01P
CC2 43 0 0.01P
CC3 44 0 0.01P
CC4 45 0 0.01P
CC5 46 0 0.01P
CC6 47 0 0.01P
CC7 48 0 0.01P
CC8 49 0 0.01P
CC9 50 0 0.01P
CCA 51 0 0.01P
CCB 52 0 0.01P
CCC 53 0 0.01P
CCD 54 0 0.01P
CCE 55 0 0.01P
CCF 56 0 0.01P
```


Voltage source name
+ node / - node
Voltage



* Positive supply voltage

```
VDD 100 0 5V
```

Transient analysis (voltage over time)
Time increment - simulation time



```
.WIDTH OUT=80
.TRAN 1NS 210NS
```


Node voltages to plot



```
*      A15   B15   Cin0 Cin15 Cout15 Sum15
.PLOT V(16) V(36) V(40) V(55) V(56) V(76)
```

```
.END
```

 16-BIT RIPPLE CARRY ADDER (SPICE) 30 JANUARY 1991
31-JAN91 10:43: 4



0. 34.000001N 68.000003N 102.0N 136.00001N 170.00001N