
 
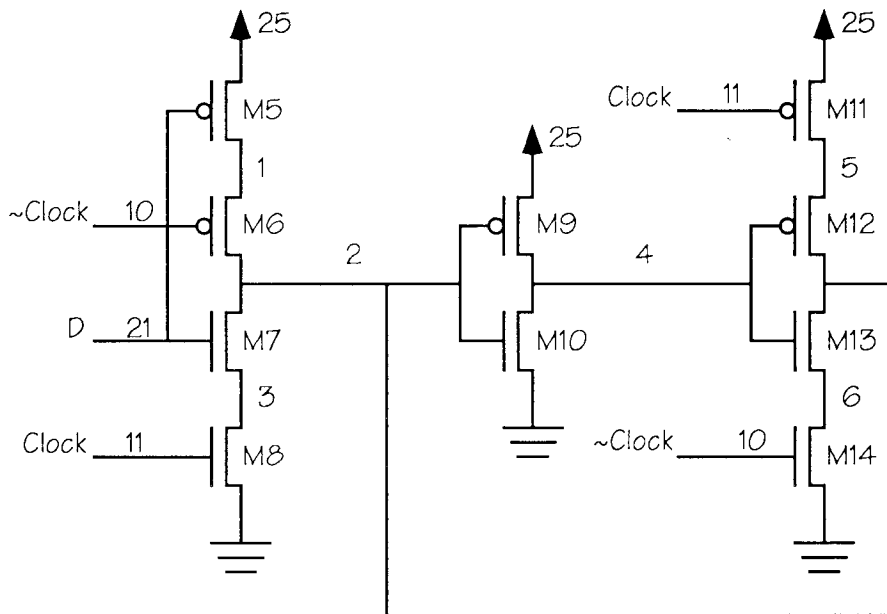


# Master slave D-latch

 

31 January 1991

## Spice example: Master / slave D-latch

```
.SUBCKT MSD 21 22 23 24 25

* Master/slave D-latch - I/O node assignments
*   D      21
*   Clock 22
*   Q      23
*   QBar   24
*   +5V    25
*   Nodes 1 2 3 4 5 6 7 8 9 12
*   CB     10
*   Cx     11
*   ND NG NS NB mname L=val W=val
M1  10 22 25 25 CMOSP L=2U W=6U
M2  10 22  0  0 CMOSN L=2U W=2U
M3  11 10 25 25 CMOSP L=2U W=6U
M4  11 10  0  0 CMOSN L=2U W=2U
M5   1 21 25 25 CMOSP L=2U W=4U
M6   2 10  1 25 CMOSP L=2U W=4U
M7   3 21  2  0 CMOSN L=2U W=2U
M8   0 11  3  0 CMOSN L=2U W=2U
M9   4  2 25 25 CMOSP L=2U W=4U
M10  4  2  0  0 CMOSN L=2U W=2U
M11  5 11 25 25 CMOSP L=2U W=4U
M12  2  4  5 25 CMOSP L=2U W=4U
M13  6  4  2  0 CMOSN L=2U W=2U
M14  0 10  6  0 CMOSN L=2U W=2U
M15  7 11 25 25 CMOSP L=2U W=6U
M16 24  4  7 25 CMOSP L=2U W=6U
M17  8  4 24  0 CMOSN L=2U W=2U
M18  0 10  8  0 CMOSN L=2U W=2U
M19 23 24 25 25 CMOSP L=2U W=8U
M20 23 24  0  0 CMOSN L=2U W=4U
M21  9 23 25 25 CMOSP L=2U W=6U
M22 24 10  9 25 CMOSP L=2U W=6U
M23 12 11 24  0 CMOSN L=2U W=3U
M24  0 23 12  0 CMOSN L=2U W=3U

.ENDS
```

## Master / slave D-latch: Spice test

```
XMSD 1 2 3 4 5 MSD
```

```
* Inputs to D-latch
```

```
VD 1 0 PWL 0N 0V 30N 0V 40N 5V 120N 5V 130N 0V  
+ 210N 0V
```

```
VCLOCK 2 0 PWL 0N 0V 60N 0V 70N 5V 90N 5V 100N 0V  
+ 150N 0V 160N 5V 180N 5V 190N 0V 210N 0V
```

```
* Capacitive load on latch outputs
```

```
CQ 3 0 0.01P
```

```
CQBAR 4 0 0.01P
```

```
* Positive supply voltage
```

```
VDD 5 0 5V
```



```
.WIDTH OUT=80
```

```
.TRAN 1NS 210NS
```

```
.PLOT V(1) V(2) V(3) V(4)
```

```
.END
```

  MASTER/SLAVE D-LATCH (SPICE) 31 JANUARY 1991  
 31-JAN91 15:25:42



42.0N 84.0N 126.0N 168.0N 210.0N

# M/S D flip-flop with reset

