 


VLSI design

Introduction to nMOS circuits


P.J. Drongowski
SandSoftwareSound.net

Inverter using pull-up resistor



- Resistor is current limiting device
- Resistor pulls output up to 5 volts
- Switch pulls output toward ground
- Voltage divider
- Must pull output below V_{th}
- Poly is about 10 ohms / square
- Need 1000 squares for 10K ohms


Inverter using enhancement pull-up

 

- Use high channel resistance
- Sheet resistance is 10Kohms/square
- Gives a compact pull-up resistor
- Voltage drop across channel is V_{th}
- V_{th} of 1 volt is typical in nMOS
- Output rises to only 4 volts




Inverter using depletion mode pull-up

$V_{dd} = +5 \text{ Volts}$

 

- Dope pull-up channel
- Implant negative ions into channel
- Sets V_{th} to -3 volts (typical)
- Channel always is turned on
- Channel provides pull-up resistance
- Pull-up must be carefully sized
- No voltage drop across channel
- Full 5 volt output

Logic gates

   


Gain


- Vout versus Vin transfer characteristics
- Gain is the slope in the middle of the curve
- Curve moves up with decreasing gain
- Curve moves down with increasing gain
- Tail of the curve must not exceed Vth (+1 volt)
- Gain is usually greater than or equal to four

- Gain =
$$\frac{L_{\text{Pull-up}} / W_{\text{Pull-up}}}{L_{\text{Pull-down}} / W_{\text{Pull-down}}}$$

- Use Spice DC analysis

 


Current consumption

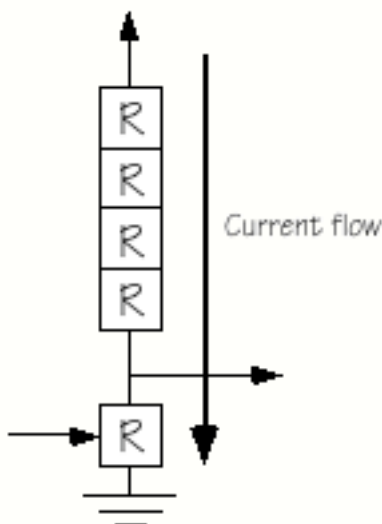


- Let R = 10K ohms
- Total resistance is 50K ohms
- Current consumption
 $I = 5 \text{ volts} / 50\text{K ohms} = 0.1 \text{ mA}$
- Power dissipation
 $P = 5 \text{ volts} \times 0.1 \text{ mA} = 0.5 \text{ mW}$


Rise time

 

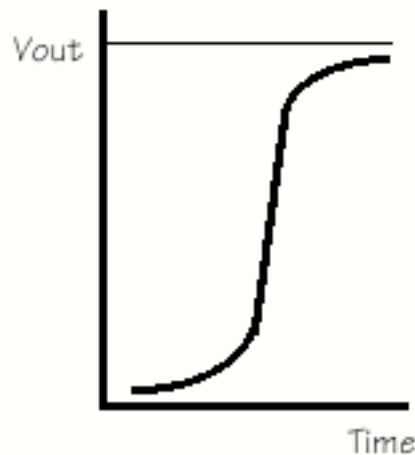
- Enhancement transistor is switched off
- $V(t) = V_{dd} \times (1 - e^{-t/RC})$
- $T_{rise} = K \times \left(\frac{L}{W}\right) \times C_{load}$ (nanoseconds)
 - L and W are length and width of pull-up transistor
 - K is a timing constant (typically 60)
 - C_{load} is the load capacitance in picofarads





Fall time

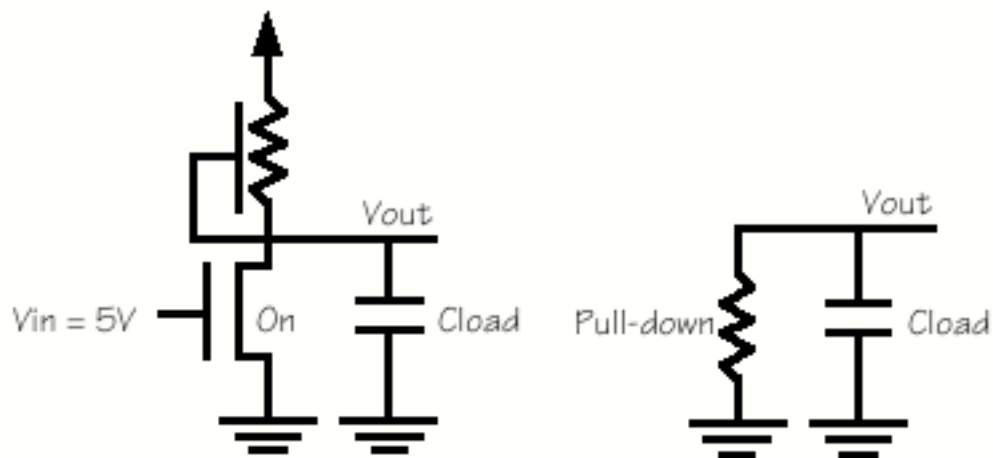

 
- Enhancement transistor is switched on
- Load capacitance is discharged through pull-down
- $T_{fall} = K \times \left(\frac{L}{W}\right) \times C_{load}$ (nanoseconds)
 - L and W are length and width of pull-down transistor
 - K is a timing constant (typically 27)
 - C_{load} is the load capacitance in picofarads




Exclusive OR

  

Superbuffers

 


Inverting superbuffers

 


Non-inverting superbuffers


Decoder (NAND form)

 

Decoder (NOR form)

 


Six transistor static memory

 

- Data lines are used for both read and write
- Drive complementary data during write to set latch
- Need sense amplifiers - long wires

Six transistor dynamic memory cell

 

- Data is stored on gate capacitors
- Charge is slowly lost (leakage current)
- Need to periodically refresh data (~ 1 msec)
- Load and refresh on alternate clock phases
- 6-transistor design good for registers, not RAM
- Use 1-transistor design for large dynamic RAM